

ITM1010

# Computer and Communication Technologies

Lecture #7

Part I: Introduction to Computer Technologies

Design of Sequential Logic Circuits

# Common sequential circuits

## ● Counters

- A digital counter is a circuit used to generate binary numbers in a specific count sequence. That sequence is mainly governed by input clock pulses, and it is repetitive as long as these clock pulses are applied. Counters serve two main functions in digital systems – counting (for example, program counter) and frequency division.


– ASYNCHRONOUS

SYNCHRONOUS


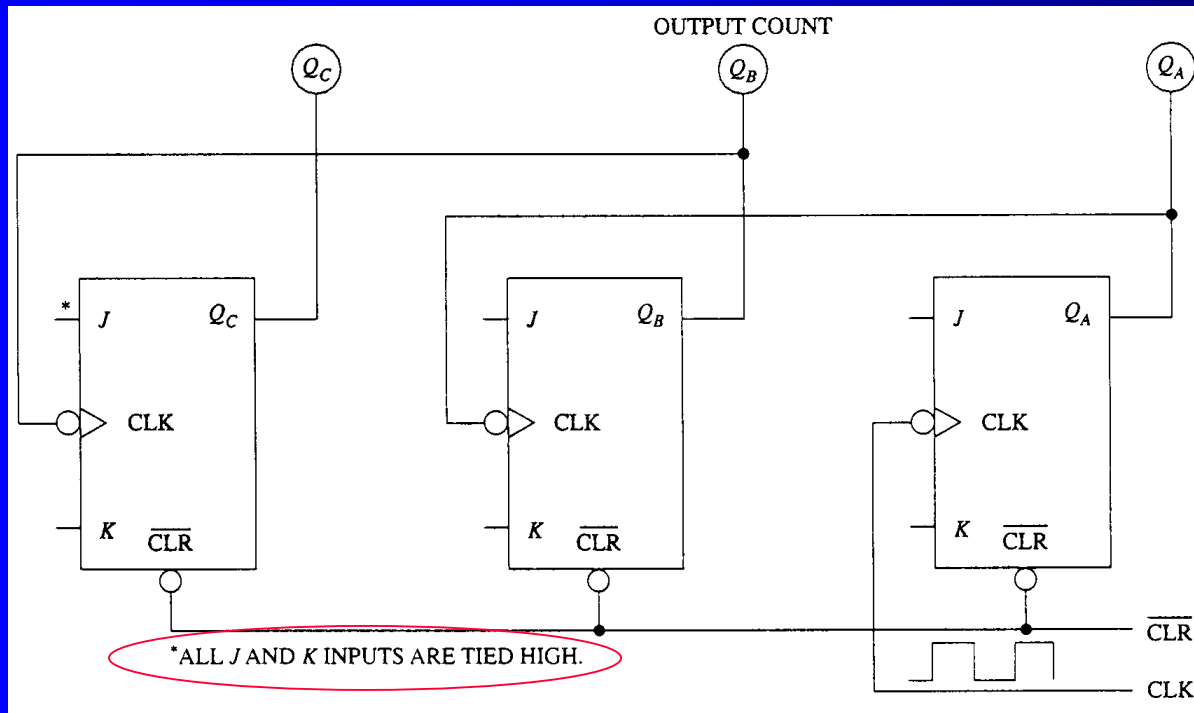
# Asynchronous Counter (Ripple Counter)

- The basic building block is a toggle flip-flop.




CLOCK	$Q_c$	$Q_B$	$Q_A$
$\overline{\text{CLR}}$	0	0	0
$t_1$	0	0	1
$t_2$	0	1	0
$t_3$	0	1	1
$t_4$	1	0	0
$t_5$	1	0	1
$t_6$	1	1	0
$t_7$	1	1	1



- It becomes down-counter if output is taken from  $\overline{Q}$




# Mod-8 Up-Counter Timing Diagram

 




# Alternative Mod-8 Up-Counter

  

# Mod-16 up counter

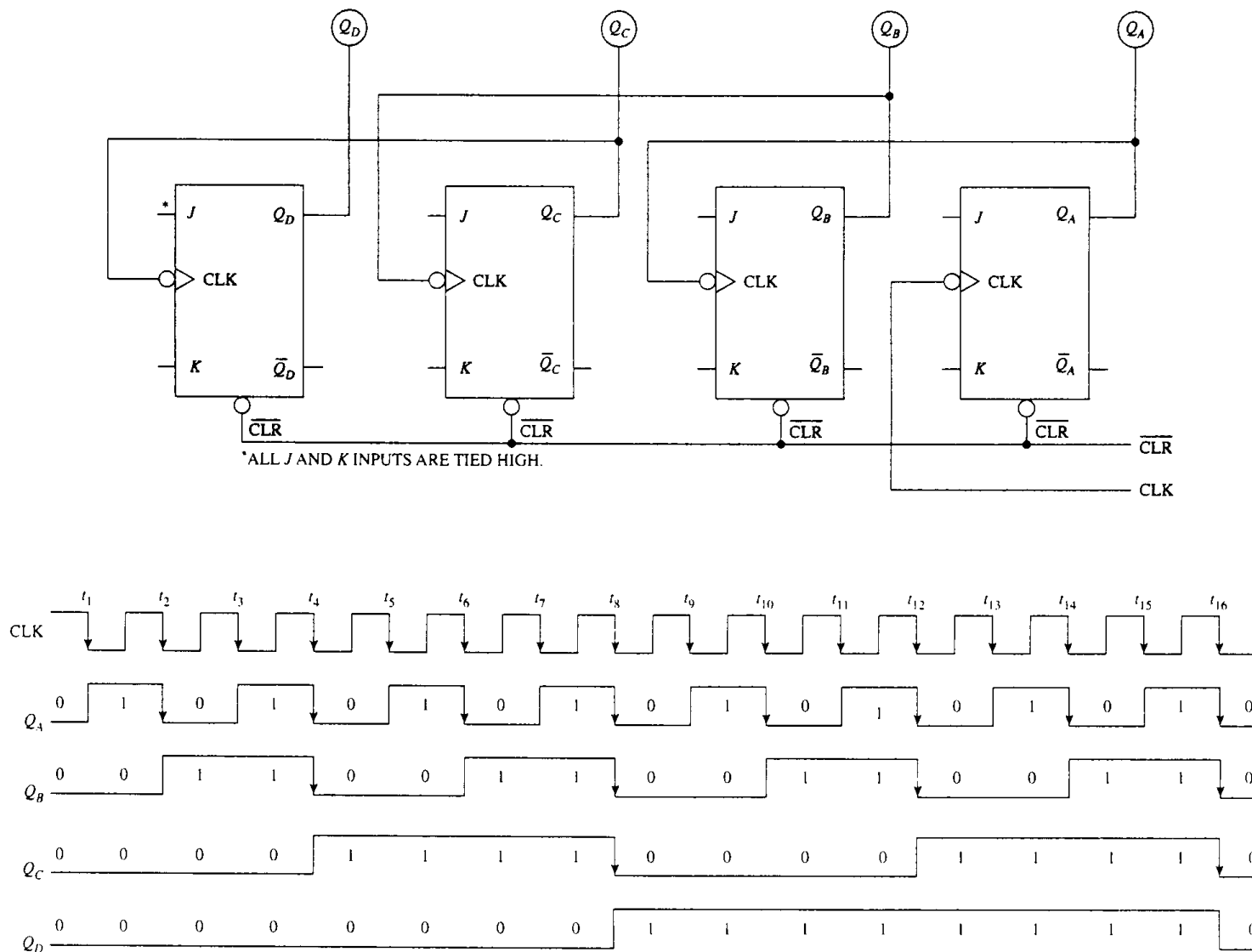

# Mod-5 counter

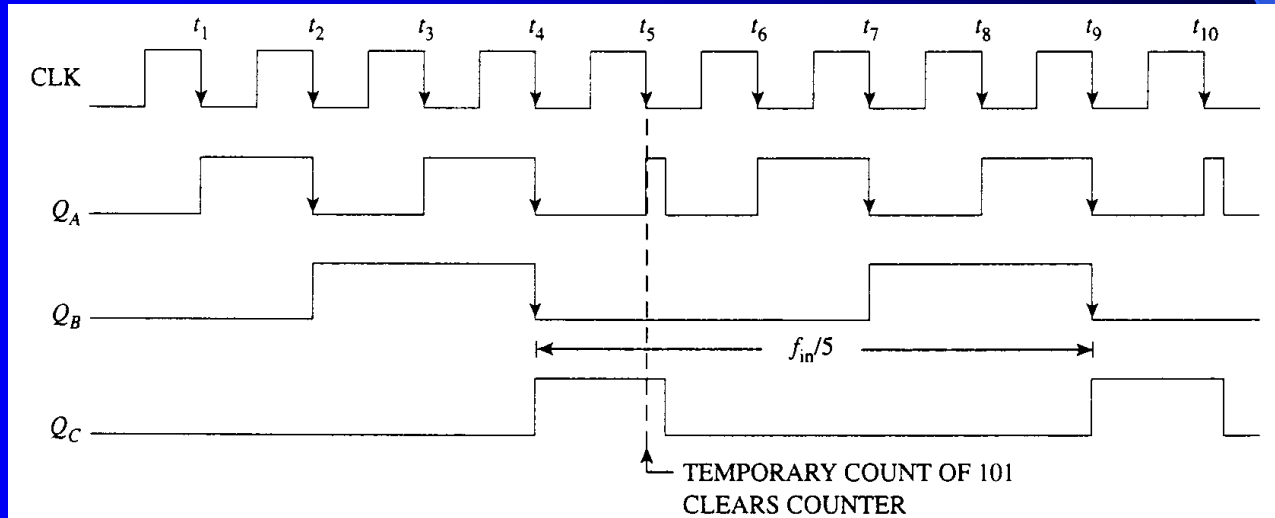 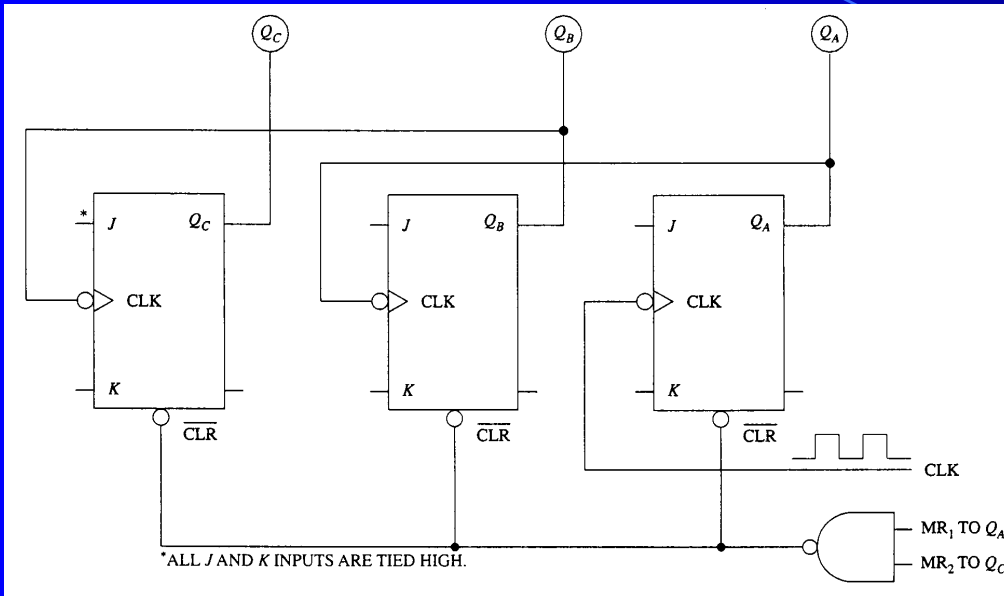


# Class exercise

- Design a mod-6 up counter








# Miscounts in asynchronous counters

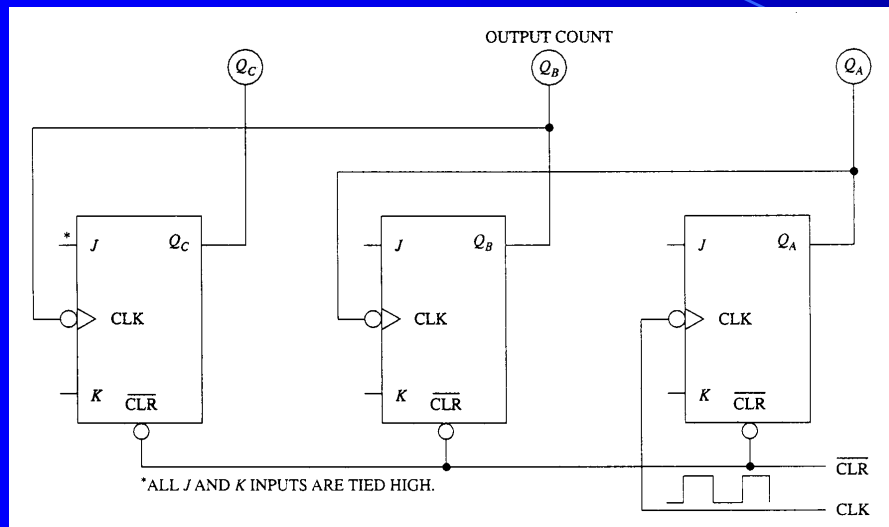

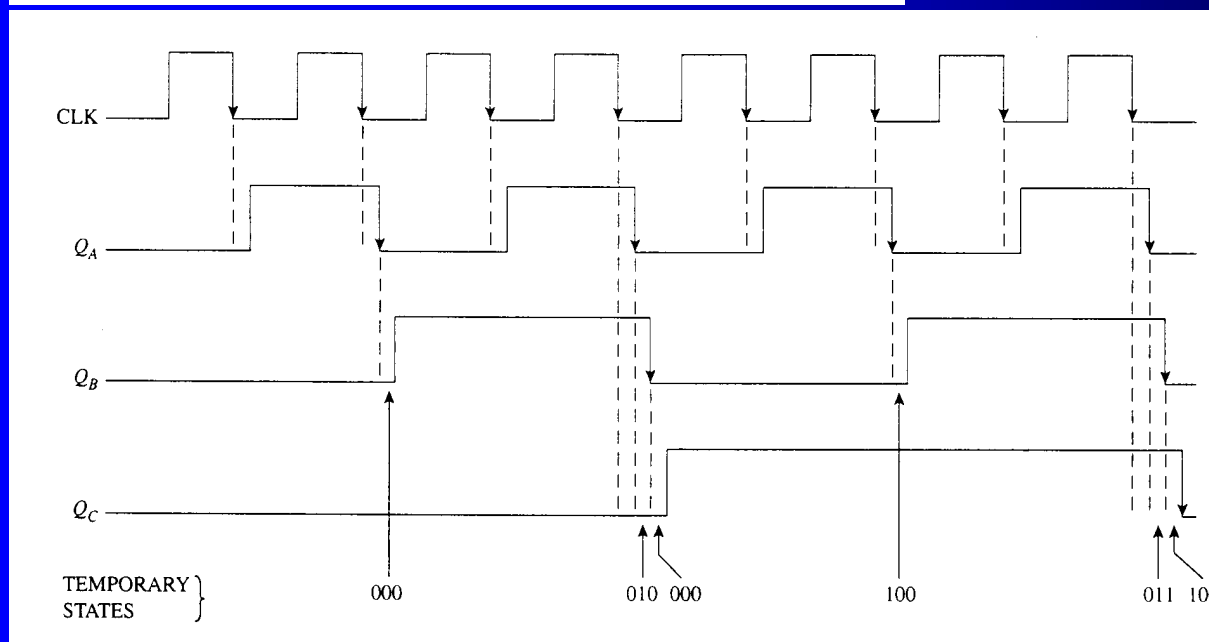- The additive propagation delays produce short duration of miscounts.
- Can be avoided in output is read synchronously.


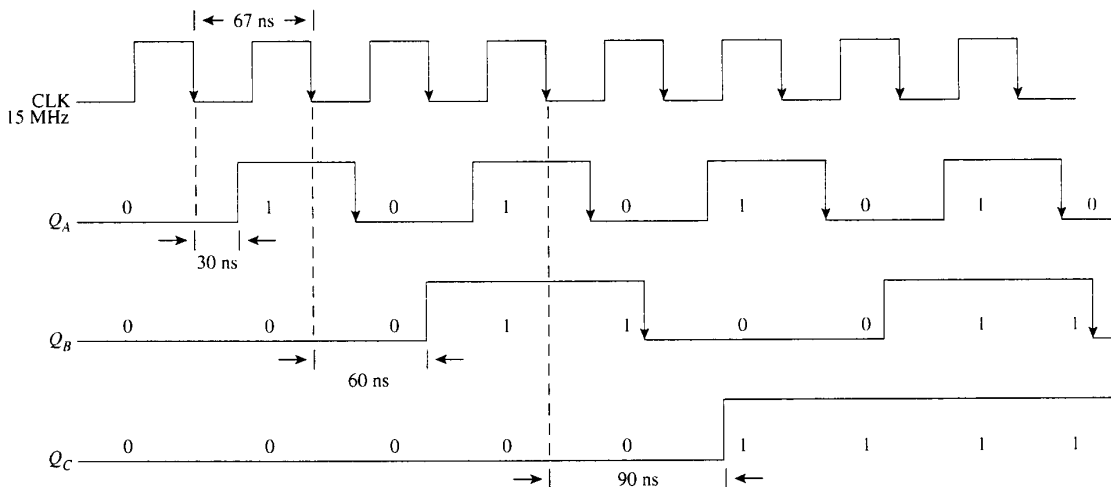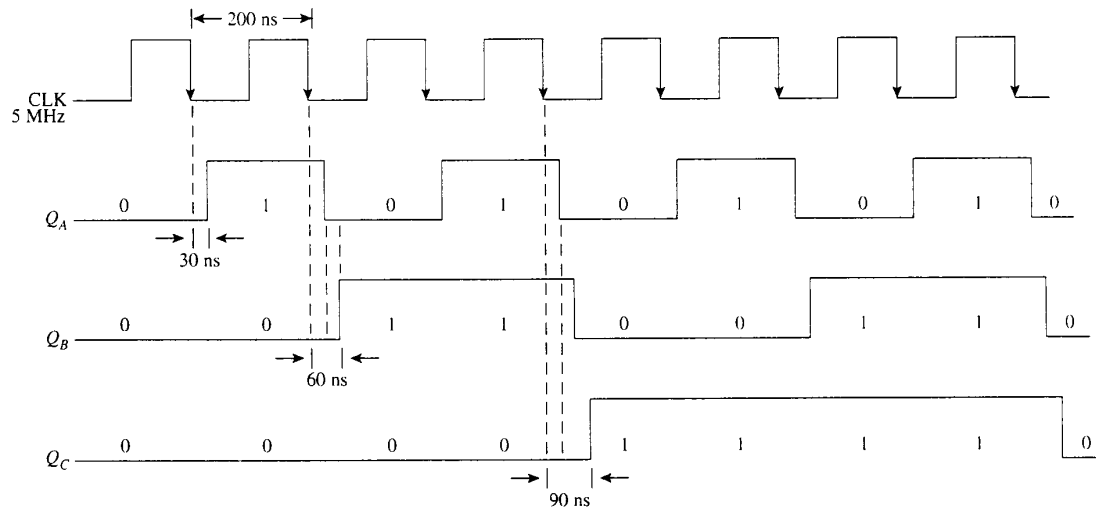
# Maximum frequency allowed in the asynchronous counters




$$f_{\max} = \frac{1}{n \tau_{ff}}$$

$n$  – number of stages

$\tau_{ff}$  – propagation delay of flip-flop
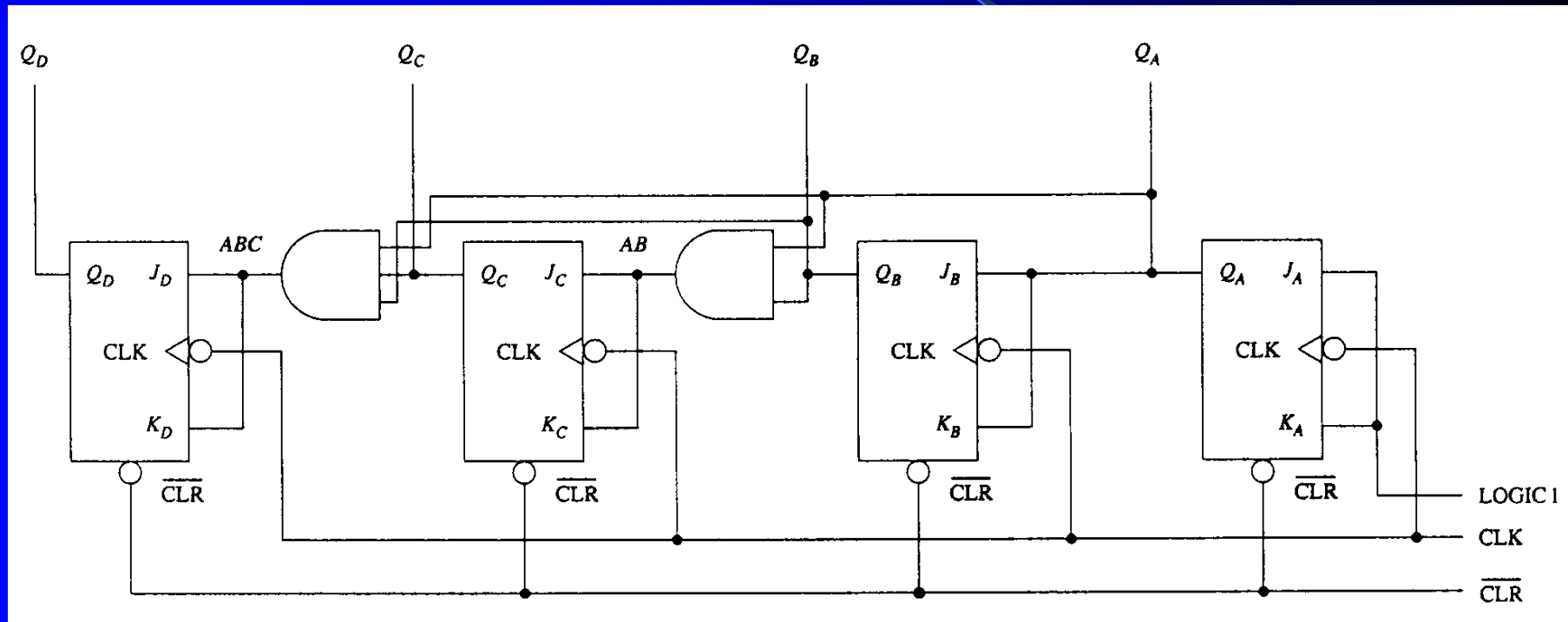
# Synchronous Counters

- All flip-flops are clocked simultaneously.



Mod-16 synchronous up-counter



# State-transition table


- QA toggles in every clock cycle;
- QB toggles when QA is 1.
- QC toggles when both QA and QB are 1.
- QD toggles when QA, QB and QC are 1.

CLOCK	$Q_D$	$Q_C$	$Q_B$	$Q_A$
CLR	0	0	0	0
$t_1$	0	0	0	1
$t_2$	0	0	1	0
$t_3$	0	0	1	1
$t_4$	0	1	0	0
$t_5$	0	1	0	1
$t_6$	0	1	1	0
$t_7$	0	1	1	1
$t_8$	1	0	0	0
$t_9$	1	0	0	1
$t_{10}$	1	0	1	0
$t_{11}$	1	0	1	1
$t_{12}$	1	1	0	0
$t_{13}$	1	1	0	1
$t_{14}$	1	1	1	0
$t_{15}$	1	1	1	1
$t_{16}$	0	0	0	0



# Synchronous mod-16 up-counter

## Timing diagram

 

↑  
No delay among  $Q_A$ ,  $Q_B$  and  $Q_C$

Maximum frequency: 
$$f_{\max} = \frac{1}{\tau_{ff}}$$




# MOD-10 Synchronous up-counter

- QA – toggle every time
- QB – toggle at A high and D low
- QC – toggle at A and B high
- QD – change high at A, B and C high but change low afterwards (A high)


	$Q_D$	$Q_C$	$Q_B$	$Q_A$
	0	0	0	0
$t_1$	0	0	0	1
$t_2$	0	0	1	0
$t_3$	0	0	1	1
$t_4$	0	1	0	0
$t_5$	0	1	0	1
$t_6$	0	1	1	0
$t_7$	0	1	1	1
$t_8$	1	0	0	0
$t_9$	1	0	0	1
$t_{10}$	0	0	0	0



# MOD-10 Synchronous up-counter

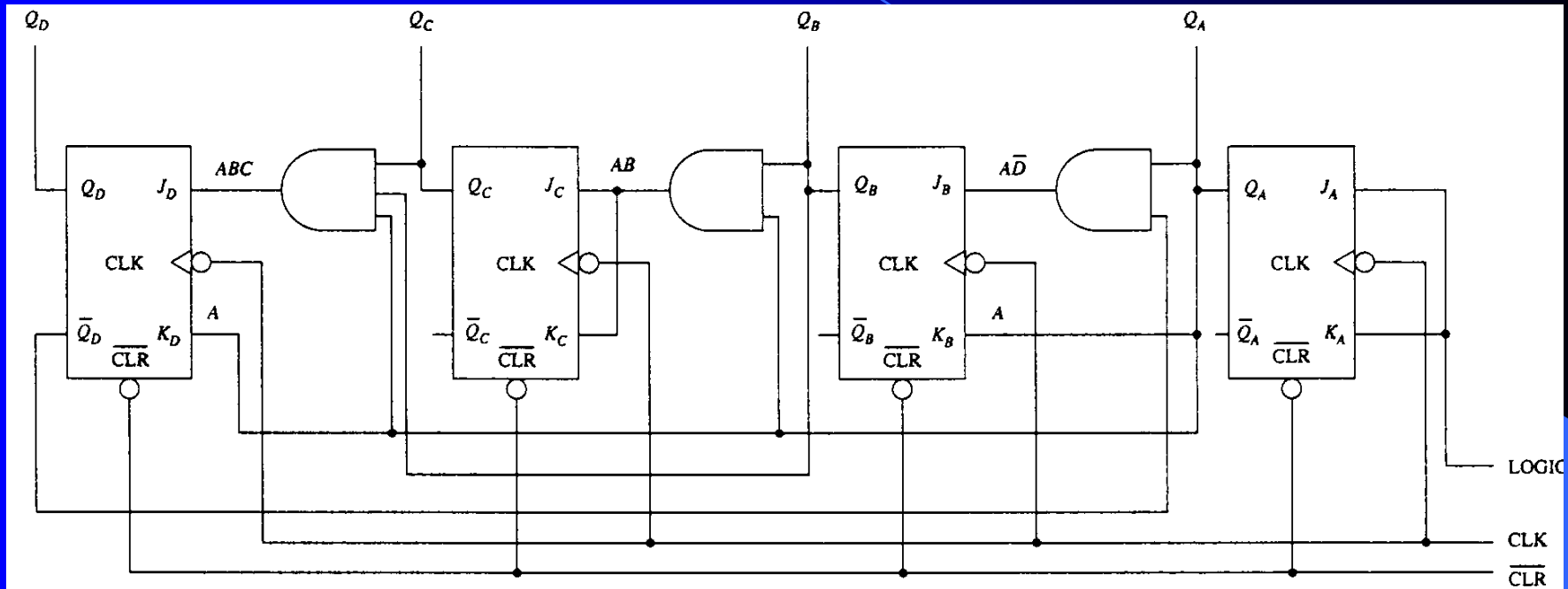

# Mod-8 synchronous down-counter

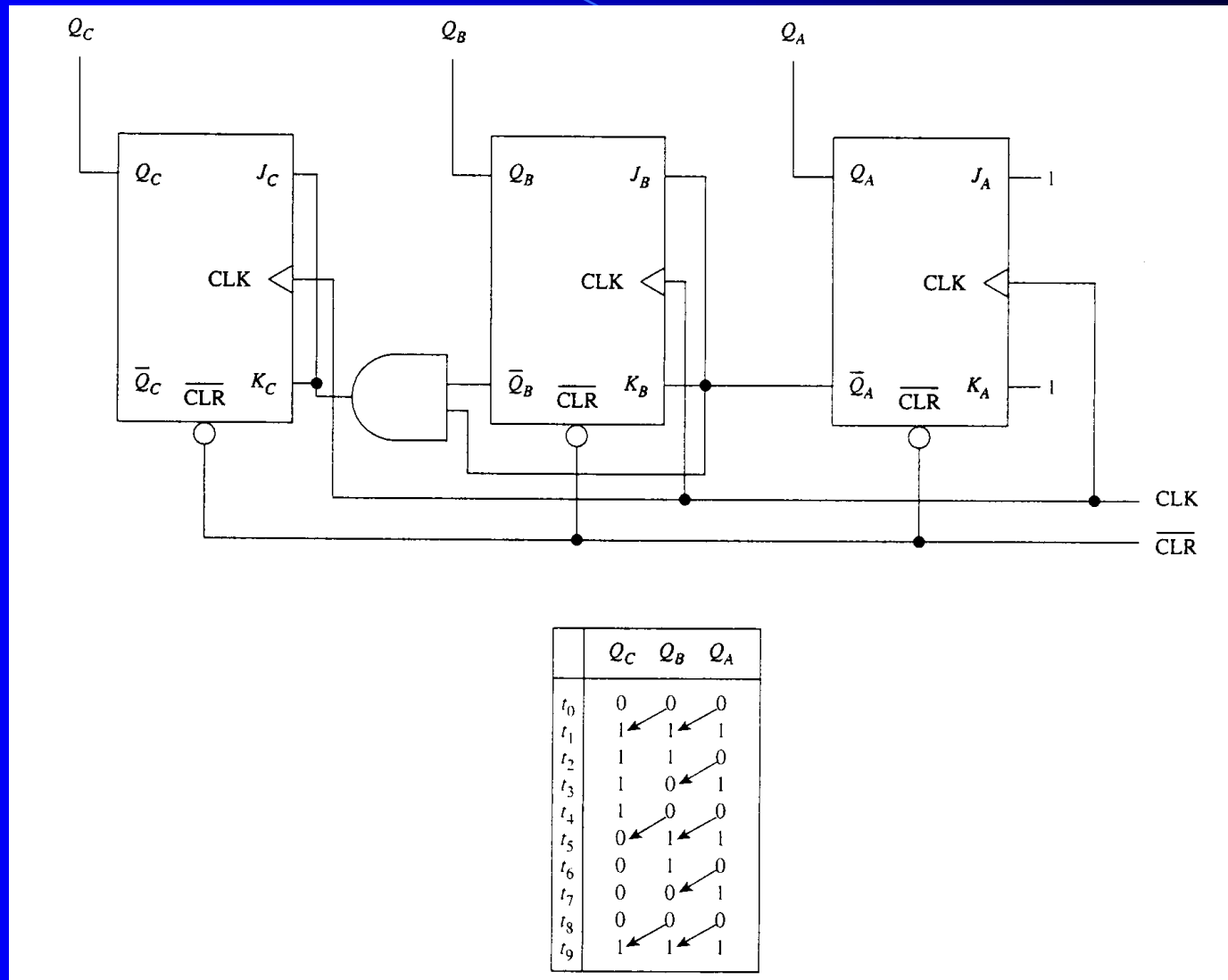



# Synchronous counter design

- Mod-6 Up-Counter Using D-flip-flops
  - Design table

<b>TABLE</b> Design Table MOD-6 (D-Type Flip-Flops)	Present State	Next State	Transition Table Data		
	$Q^n$	$Q^{n+1}$	$Q_C$	$Q_B$	$Q_A$
	$Q_C Q_B Q_A$	$Q_C Q_B Q_A$	$D_C$	$D_B$	$D_A$
	000 001 010 011 100 101	001 010 011 100 101 000	0 0 0 1 1 0	0 1 1 0 0 0	1 0 1 0 1 0



# Mod-6 up-counter

– K-maps

DA

$Q_C Q_B$		$Q_A$	
		0	1
00		1	0
01		1	0
11		X	X
10		1	0

$D_A = \bar{A}$

DB

$Q_C Q_B$		$Q_A$	
		0	1
00		0	1
01		1	0
11		X	X
10		0	0


$D_B = \bar{A}B + A\bar{B}\bar{C}$

DC

$Q_C Q_B$		$Q_A$	
		0	1
00		0	0
01		0	1
11		X	X
10		1	0

$D_C = AB + \bar{A}C$

# Mod-6 up-counter


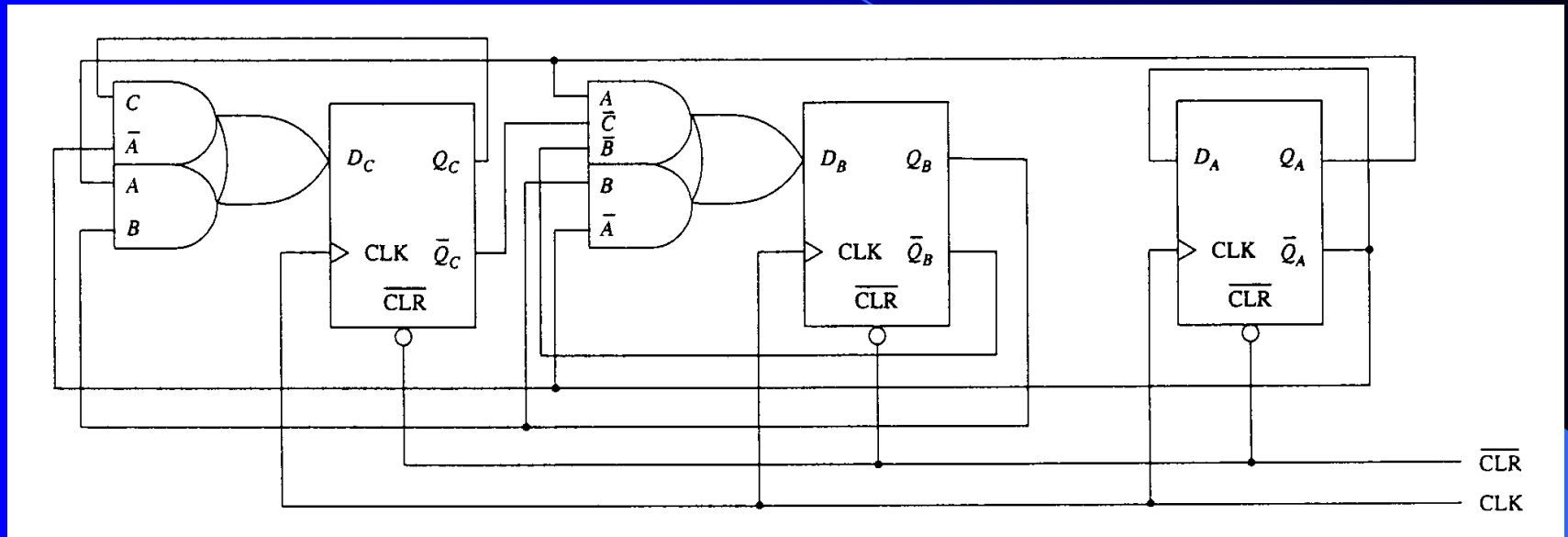


# Final Design



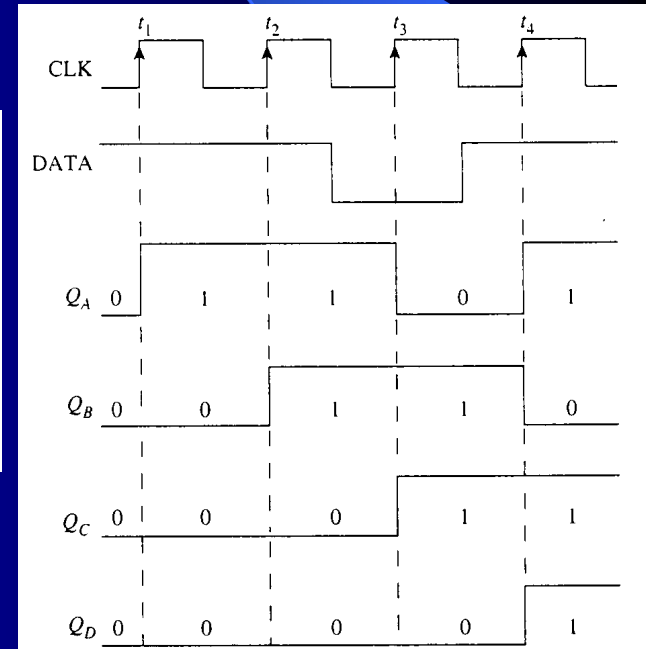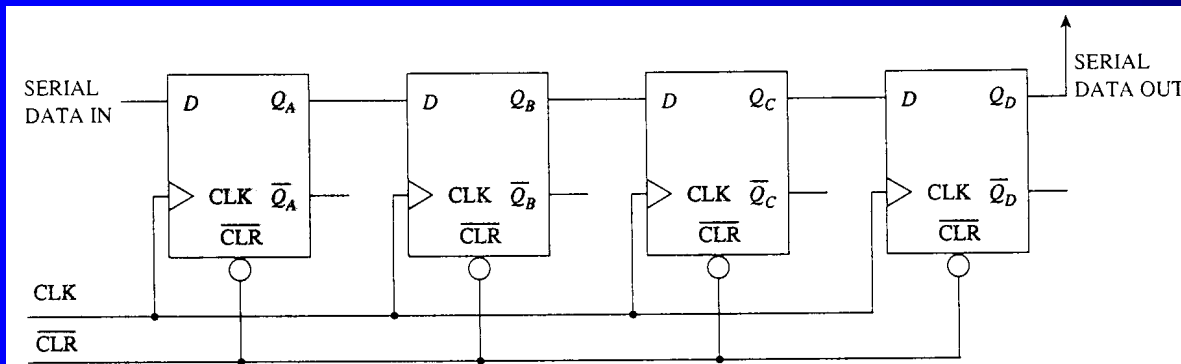
# REGISTERS

- A group of latches or flip-flops used to store, transfer, or shift data
- Serial Shift Register
  - Data is clocked into the register bit by bit


 
# RING COUNTER


- The counter is a shift register that has its output connected back to its own input


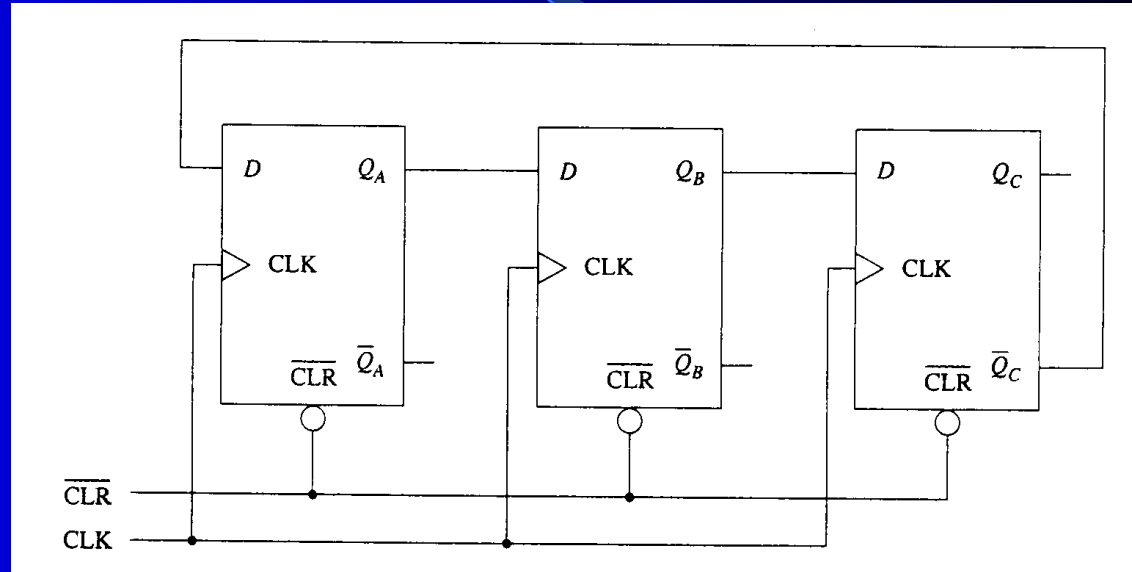
# JONHSON COUNTER

- Each bit is toggled in turn
- Mod-6

- 000
- 100
- 110
- 111
- 011
- 001
- 000




- With its unique bit pattern, any sequence can be detected with a 2-input gate



 
# MULTIPLY/DIVIDE REGISTER

- A left shift operation multiplies a binary number by a factor of 2
- A right shift operation divides a binary number by a factor of 2



# Pseudo-random sequence generator

 

$Q_A$	$Q_B$	$Q_C$	$Q_D$
0	0	0	0
1	0	0	0
0	1	0	0
0	0	1	0
1	0	0	1
1	1	0	0
0	1	1	0
1	0	1	1
0	1	0	1
1	0	1	0
1	1	0	1
1	1	1	0
1	1	1	1
0	1	1	1
0	0	1	1
0	0	0	1
1	0	0	0

INVALID CONDITION

